

CIRCUITOS LÓGICOS PROGRAMABLES

# GENERADOR DE SEÑALES SENOIDALES




---

Alumno: Lucas Orsi  
Cohorte: 14va  
Universidad de Buenos Aires




# Introducción

# Diagrama General del Sistema

 


# Esquemático

## Esquemático General

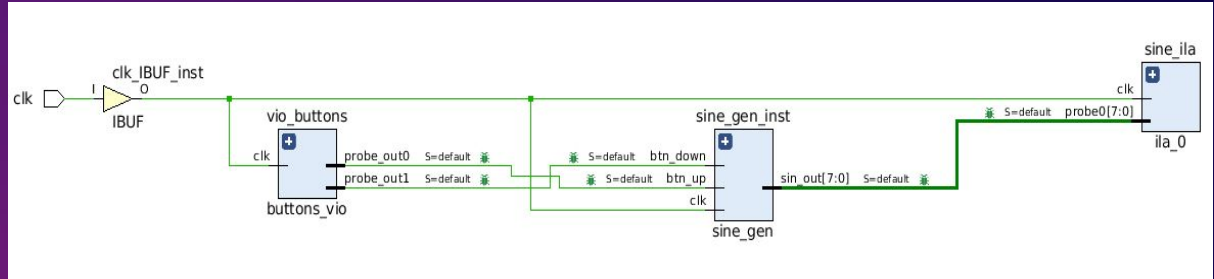


## Generador de Senoidales

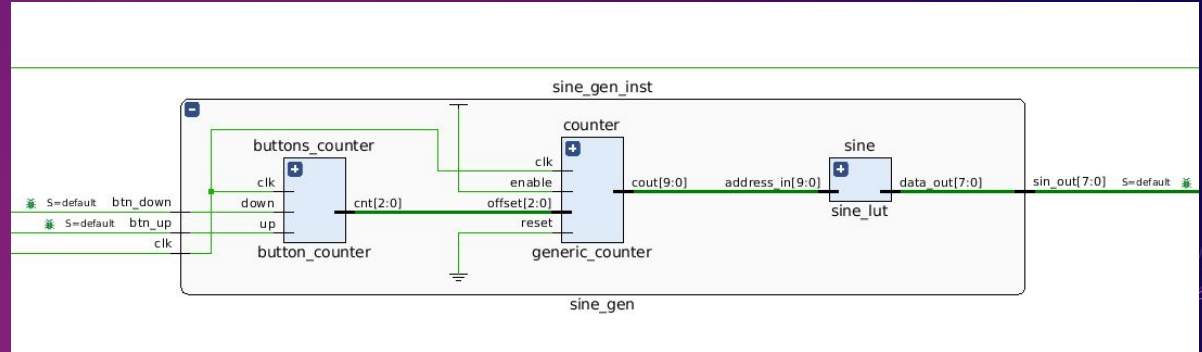




# Bloques Funcionales

# Manejador de Botones

 


```
process(clk)
begin
  if rising_edge(clk) then
    if up = '1' and last_up = '0'
      and internal_counter < N then
      internal_counter <= internal_counter + 1;
    end if;
    if down = '1' and last_down = '0'
      and internal_counter > 0 then
      internal_counter <= internal_counter - 1;
    end if;
    last_up <= up;
    last_down <= down;
  end if;
end process;
cnt <= std_logic_vector(internal_counter);
```

# Manejador de Botones

 

```
architecture button_counter_tb_arch of button_counter_tb is
    component button_counter is
        generic(N: natural := 2; N_BITS: natural := 2);
        port(
            clk:    in std_logic;
            up:     in std_logic;
            down:   in std_logic;
            cnt:    out std_logic_VECTOR (N_BITS - 1 downto 0)
        );
    end component;
```


# Contador Principal

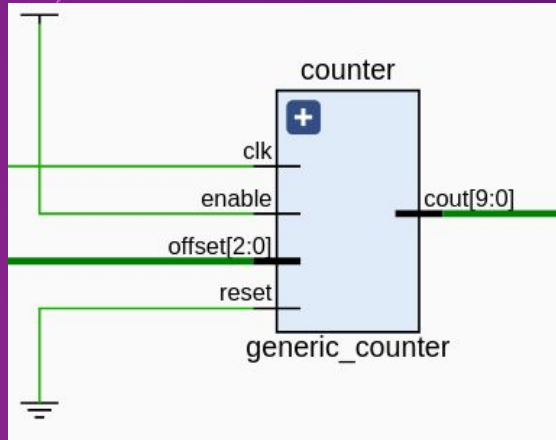


```
process (clk, reset) begin
    if (reset = '1') then
        count <= (others=>'0');
    elsif (rising_edge(clk)) then
        if (enable = '1') then
            count <= count + unsigned(offset) + 1;
        end if;
    end if;
end process;
cout <= std_logic_vector(count);
```



# Contador Principal

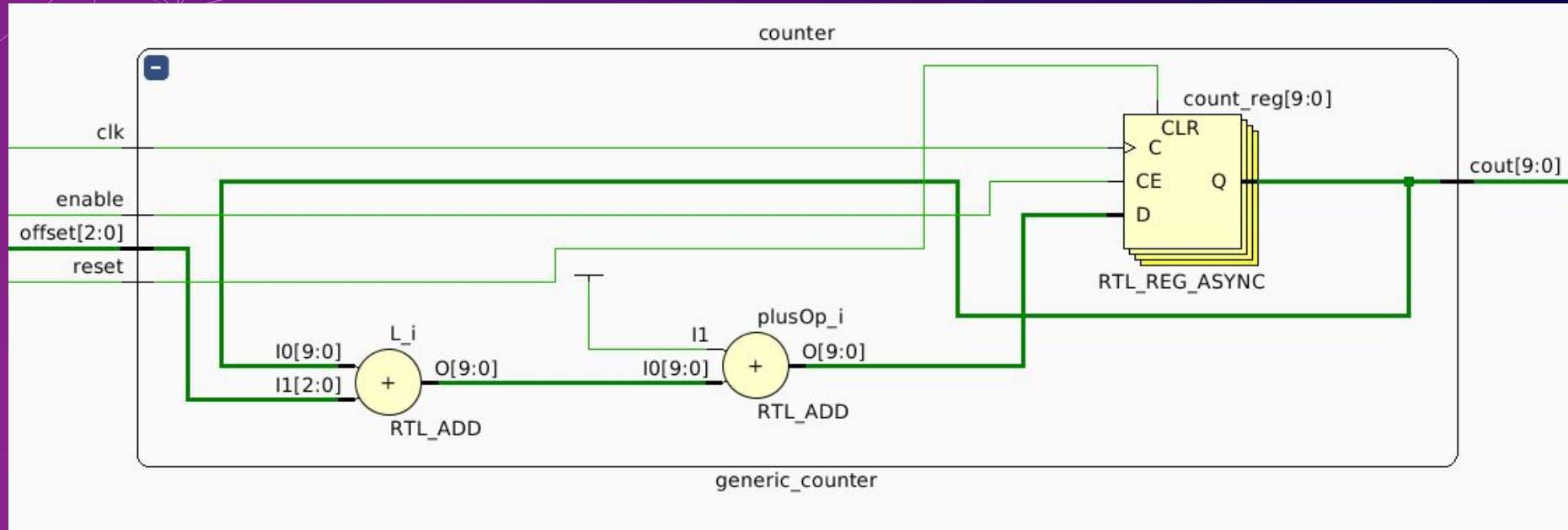


# Contador Principal

 

```
component generic_counter is
  generic(OUTPUT_WIDTH: natural := 8; COUNT_OFFSET_WIDTH: natural := 3);
  port (
    cout    :out std_logic_vector (OUTPUT_WIDTH - 1 downto 0);
    enable  :in  std_logic;
    clk     :in  std_logic;
    offset  :in  std_logic_vector(COUNT_OFFSET_WIDTH - 1 downto 0);
    reset   :in  std_logic
  );
end component generic_counter;
```


# Tabla de Señal

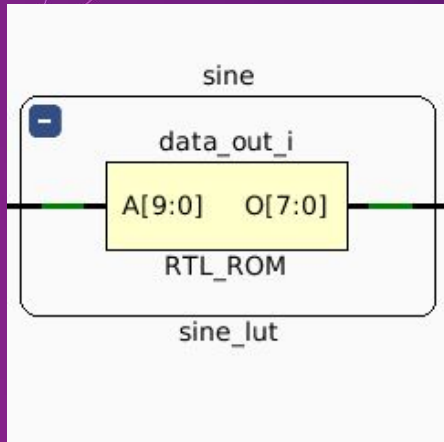


```
process(address_in) is
begin
    case address_in is
        when "0000000000" => data_out <= "01111111";
        when "0000000001" => data_out <= "10000000";
        ...
        when "1111111110" => data_out <= "01111111";
        when "1111111111" => data_out <= "01111111";
        when others => data_out <= (others => '0');
    end case;
end process;
```

# Simulación del Sistema

## Botón “Up”

 

## Botón “Up” y luego “Down”

 



# Prueba en Hardware






# Análisis de Resultados

# Reporte de Utilización


Utilization (7.77%)

 

ILA    DBG Hub    Sine Gen Instance    VIO Buttons



# Senoidales Obtenidas

 

# Herramientas Personalizadas

```
$ python3 tools/vhdlutils.py --help


usage: vhdlutils.py [-h] [--time TIME] [--compile-only] component

Compile and simulate VHDL sources.

positional arguments:
  component            Component whose testbench will be simulated

optional arguments:
  -h, --help            show this help message and exit
  --time TIME           simulation stoptime in nanoseconds
  --compile-only        does not run any simulation
```

 **Compilación y  
Simulación de Fuentes**



**Generación de Tablas de  
Senoidales en VHDL**



```
$ python3 tools/sine_table_gen.py

begin
  case address is
    when "0000000000" => result <= "01111111"; -- 0x7f
    when "0000000001" => result <= "10000000"; -- 0x80
    when "0000000010" => result <= "10000001"; -- 0x81
    when "0000000011" => result <= "10000010"; -- 0x82
    when "0000000100" => result <= "10000011"; -- 0x83
    when "0000000101" => result <= "10000011"; -- 0x83
    when "0000000110" => result <= "10000100"; -- 0x84
    ...
```

# Gracias!



Preguntas?

